

VHDL Modeling for Synthesis

Arithmetic Functions and IEEE numeric_std package

Text: 12.6.5, 12.6.9, 12.6.10

Synthesizing arithmetic circuits

(12.6.5, 12.6.9, 12.6.10)

- ▶ Synthesis tool recognizes overloaded operators and generates corresponding circuits:

“+”, “-”, “*”, and “abs” (add, sub, multiply, abs. value)

- ▶ Special operations:

“+1”, “-1”, unary “-” (increment, decrement, negate)

- ▶ Relational Operators:

“=”, “/=", “<”, “>”, “<=”, “>=

- ▶ Use ranged integers instead of unbound to minimize generated logic.

signal i : integer range 0 to 15; --4-bit number



Leonardo restrictions

- ▶ Non-integer data types (`std_logic_vector`) require operator overloading to produce arithmetic circuits
 - ▶ A function must be supplied to produce a result for operands having designated data types
 - ▶ IEEE library packages define arithmetic functions for certain combinations of data types
- ▶ Multiply operator “*” will produce a multiplier, but more efficient technology-specific modules may be better.
- ▶ Divide operator “/” only works if dividing by a power of 2, unless using a technology-specific module



Behavioral model of an adder

entity adder is

```
port ( a:      in integer; -- abstract data type
      b:      in integer;
      sum: out integer);
```

end adder ;

architecture behave of adder is

```
begin
```

```
    sum <= a + b; --synthesis produces adder circuit
```

```
end;
```



Adders/subtractors automatically generated for integer data

variable a,b,c: integer;

c := a + b; -- produces 32-bit adder (signed)

variable a,b,c: integer range 0 to 255;

c := a + b; -- produces 8-bit adder (unsigned)

Constant operands result in reduced logic by removing logic due to hard-wired values.

Ex: c := a + 5;



IEEE Std. 1076.3 Synthesis Libraries

(12.6.5, 12.6.9, 12.6.10)

- ▶ **Support for arithmetic models (preferred):**
 - ▶ **ieee.numeric_std** (ieee library package)
 - ▶ defines UNSIGNED and SIGNED as arrays of std_logic
 - type SIGNED is array(NATURAL range <>) of STD_LOGIC;
 - type UNSIGNED is array(NATURAL range <>) of STD_LOGIC;
 - ▶ defines standard arithmetic/relational operators on these types
- ▶ **Lesser-used packages:**
 - ▶ **ieee.numeric_bit**
 - ▶ same as above except SIGNED/UNSIGNED are arrays of type bit
 - ▶ **ieee.std_logic_arith** (*from Synopsis*)
 - ▶ Non-standard predecessor of numeric_std/numeric_bit



NUMERIC_STD package contents

- ▶ Arithmetic functions: + - * / rem mod
 - ▶ Combinations of operands for which operators are defined:
 - ▶ SIGNED + SIGNED return SIGNED
 - ▶ SIGNED + INTEGER return SIGNED
 - ▶ INTEGER + SIGNED return SIGNED
 - ▶ SIGNED + STD_LOGIC return SIGNED
 - ▶ PLUS: above combinations with UNSIGNED and NATURAL
- ▶ Other operators for SIGNED/UNSIGNED types:
 - ▶ Relational: = /= < > <= >=
 - ▶ Shift/rotate: sll, srl, sla, sra, rol, ror
 - ▶ Maximum(a,b), Minimum(a,b)
- ▶ Convert between types:
 - ▶ TO_INTEGER(SIGNED), TO_INTEGER(UNSIGNED)
 - ▶ TO_SIGNED(INTEGER,#bits), TO_UNSIGNED(NATURAL,#bits)
 - ▶ RESIZE(SIGNED or UNSIGNED,#bits) – changes # bits in the vector



RTL models of arithmetic functions

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  UNSIGNED(3 downto 0) ;
           mySum : out UNSIGNED(3 downto 0) ) ;
end Adder4;

architecture Behave_B of Adder4 is
begin
    mySum <= in1 + in2; -- overloaded '+' operator
end Behave_B;
```



Conversion of “closely-related” types

- ▶ **STD_LOGIC_VECTOR, SIGNED, UNSIGNED:**
 - ▶ All three types are arrays of STD_LOGIC elements
 - ▶ Example: Consider how to interpret “1001”
 - ▶ STD_LOGIC_VECTOR: simple array of four bits
 - ▶ SIGNED: array of bits representing the number -7 (2's complement #)
 - ▶ UNSIGNED: array of bits representing the number 9 (unsigned #)
- ▶ Vectors of the same element types may be “converted” (re-typed/re-cast) from one type to another

```
signal A: std_logic_vector(3 downto 0) := “1001”;
signal B: signed(3 downto 0);
signal C: unsigned(3 downto 0);
B <= signed(A);           -- interpret A value “1001” as number -7
C <= unsigned(A);         -- interpret A value “1001” as number 9
A <= std_logic_vector(B); -- interpret B as bit pattern “1001”
```



Conversion of “closely-related” types

For arrays of same dimension, *having elements of same type*

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  STD_LOGIC_VECTOR(3 downto 0) ;
          mySum : out STD_LOGIC_VECTOR(3 downto 0) ) ;
end Adder4;

architecture Behave_B of Adder4 is
begin
    mySum <=
        STD_LOGIC_VECTOR( SIGNED(in1) + SIGNED(in2) );
end Behave_B;
```

Interpret STD_LOGIC_VECTOR as SIGNED
for function: SIGNED = SIGNED + SIGNED.

Interpret SIGNED result as STD_LOGIC_VECTOR.



Example – binary counter

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
use IEEE.NUMERIC_STD.all;
```

```
ENTITY counter IS
```

```
    port( Q: out std_logic_vector(3 downto 0);
```

```
        ....
```

```
END counter;
```

```
ARCHITECTURE behavior OF counter IS
```

```
    signal Qinternal: unsigned(3 downto 0);
```

```
begin
```

```
    Qinternal <= Qinternal + 1;           -- “+” defined in numeric_std**
```

```
    Q <= std_logic_vector(Qinternal);    -- re-type unsigned as std_logic_vector
```

```
    ....
```

```
** numeric_std defines “+” function: UNSIGNED = UNSIGNED + NATURAL
```



Using a “variable” to describe sequential behavior within a process

-- assume Din and Dout are std_logic_vector

-- and numeric_std package is included

cnt: process(clk)

 variable count: integer; -- internal counter state

 begin -- valid only within a process

 if clk='1' and clk'event then

 if ld='1' then

 count := to_integer(unsigned(Din)); --update immediately

 elsif cnt='1' then

 count := count + 1; --update immediately

 end if;

 end if;

 Dout <= std_logic_vector(to_unsigned(count,32)); --**schedule** ΔDout

 end process;



Using a “variable” to describe sequential behavior within a process

-- assume Din and Dout are std_logic_vector

-- and numeric_std package is included

cnt: process(clk)

 variable count: integer; -- internal counter state

 begin -- valid only within a process

 if clk='1' and clk'event then

 if ld='1' then

 count := to_integer(unsigned(Din)); --update immediately

 elsif cnt='1' then

 count := count + 1; --update immediately

 end if;

 end if;

 Dout <= std_logic_vector(to_unsigned(count,32)); --**schedule** ΔDout

 end process;



Add/Sub “Accumulator”

-- result_t , xin, addout are UNSIGNED

with addsub select – combinational add/sub

```
addout <= (xin + result_t) when '1',  
          (xin - result_t) when '0',  
          (others => '-') when others;
```

process (clr, clk) begin -- register part

```
    if (clr = '0') then
```

```
        result_t <= (others => '0');
```

```
    elsif rising_edge(clk) then
```

```
        result_t <= addout;
```

```
    end if;
```

```
end process;
```

-- “when others” creates exhaustive list of choices



Simplified “accumulator” model

-- signal addsub eliminated – circuit will be the same


```
process (clr, clk) begin
    if (clr = '0') then
        result_t <= (others => '0');
    elsif rising_edge(clk) then
        case addsub is
            when '1'      => result_t <= (xin + result_t);
            when '0'      => result_t <= (xin - result_t);
            when others => result_t <= (others => '-');
        end case;
    end if;
end process;
```



Multiple adder structures


$z \leq a + b + c + d;$

-- 3 adders stacked 3 deep

 


$z \leq (a + b) + (c + d);$

-- 3 adders stacked 2 deep

 

Resource sharing for mutually-exclusive operations
 
```
process (a,b,c,test) begin  
  if (test=TRUE) then  
    o <= a + b ; -- either this evaluates  
  else  
    o <= a + c ; -- or this evaluates  
  end if ;  
end process ;  
-- Leonardo generates two adders & one mux
```



Equivalent model

```
process (a,b,c,test) begin  
    variable tmp : integer range 0 to 255 ;  
begin  
    if (test=TRUE) then -- mux will select b or c  
        tmp := b ;  
    else  
        tmp := c ;  
    end if ;  
    o <= a + tmp ; -- mux output added to a  
end process ;  
-- one adder and one mux generated
```

